

Filippos Symeonidis 20200092

This project is about optimized digital circuit which accepts a 4-bit binary number as input and outputs the corresponding number encoded in the Gray and BCD5421 formats. The circuit has 4 bits (ABCD) representing the binary number input and a 5th selection bit (E) to select whether to output in Gray (E = 1) or BCD5421 (E = 0) encoding. The first four outputs represent the binary number, while the fifth shows if an error occurred or not. The encoder only accepts numbers between 0 and 9, anything beyond that is regarded as an error. For each of the five outputs (QRSTU), the creation of the digital circuit will be explained step by step.

## Truth Tables:

[illegible]

Binary					BCD (5421)				
A	B	C	D	E	Q	R	S	T	U
0	0	0	0	0	0	0	0	0	0

0	0	0	1	0	0	0	0	1	0
0	0	1	0	0	0	0	1	0	0
0	0	1	1	0	0	0	1	1	0
0	1	0	0	0	0	1	0	0	0
0	1	0	1	0	1	0	0	0	0
0	1	1	0	0	1	0	0	1	0
0	1	1	1	0	1	0	1	0	0
1	0	0	0	0	1	0	1	1	0
1	0	0	1	0	1	1	0	0	0
1	0	1	0	0	X	X	X	X	1
1	0	1	1	0	X	X	X	X	1
1	1	0	0	0	X	X	X	X	1
1	1	0	1	0	X	X	X	X	1
1	1	1	0	0	X	X	X	X	1
1	1	1	1	0	X	X	X	X	1

## Karnaugh Maps:

Q Karnaugh Map:

AB/CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

Grey Code E=1

AB/CD	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

BCD (5421) E=0

$$Q = BC\bar{E} + BD\bar{E} + A$$

$$Q = B\bar{E}(C + D) + A$$

R Karnaugh Map:

AB/CD	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

Grey Code E=1

AB/CD	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	X	X	X	X
10	0	1	X	X

BCD (5421) E=0

$$R = \bar{A}BC\bar{D} + \bar{A}\bar{B}E + \bar{A}BE + \bar{A}\bar{B}D$$

$$R = \bar{A}B(\bar{C}\bar{D} + E) + \bar{A}\bar{B}(E + D)$$

S Karnaugh Map:

AB/CD	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

Grey Code E=1

AB/CD	00	01	11	10
00	0	0	1	1
01	0	0	1	0
11	X	X	X	X
10	1	0	X	X

BCD (5421) E=0

$$S = \overline{B}\overline{D}\overline{E} + \overline{C}\overline{D}\overline{E} + \overline{B}\overline{C}E + \overline{B}C$$

$$S = \overline{E}(\overline{B}\overline{D} + \overline{C}\overline{D}) + \overline{B}\overline{C}E + \overline{B}C$$

T Karnaugh Map:

AB/CD	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

Grey Code E=1

AB/CD	00	01	11	10
00	0	1	1	0
01	0	0	0	1
11	X	X	X	X
10	1	0	X	X

BCD (5421) E=0

$$T = \overline{A}\overline{B}\overline{D}\overline{E} + \overline{A}\overline{D}\overline{E} + \overline{B}\overline{C}\overline{D} + \overline{C}\overline{D}E + \overline{C}\overline{D}\overline{E}$$

$$T = \overline{E}(\overline{A}\overline{B}\overline{D} + \overline{A}\overline{D}) + \overline{D}(\overline{B}\overline{C} + \overline{C}E) + \overline{C}\overline{D}E$$

U Karnaugh Map:

AB/CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

Grey Code E=1


AB/CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	1

BCD (5421) E=0


$$U = \overline{A}\overline{C}\overline{E} + \overline{A}\overline{B}\overline{E}$$

$$U = \overline{A}\overline{E}(\overline{C} + \overline{B})$$


## The Circuit:

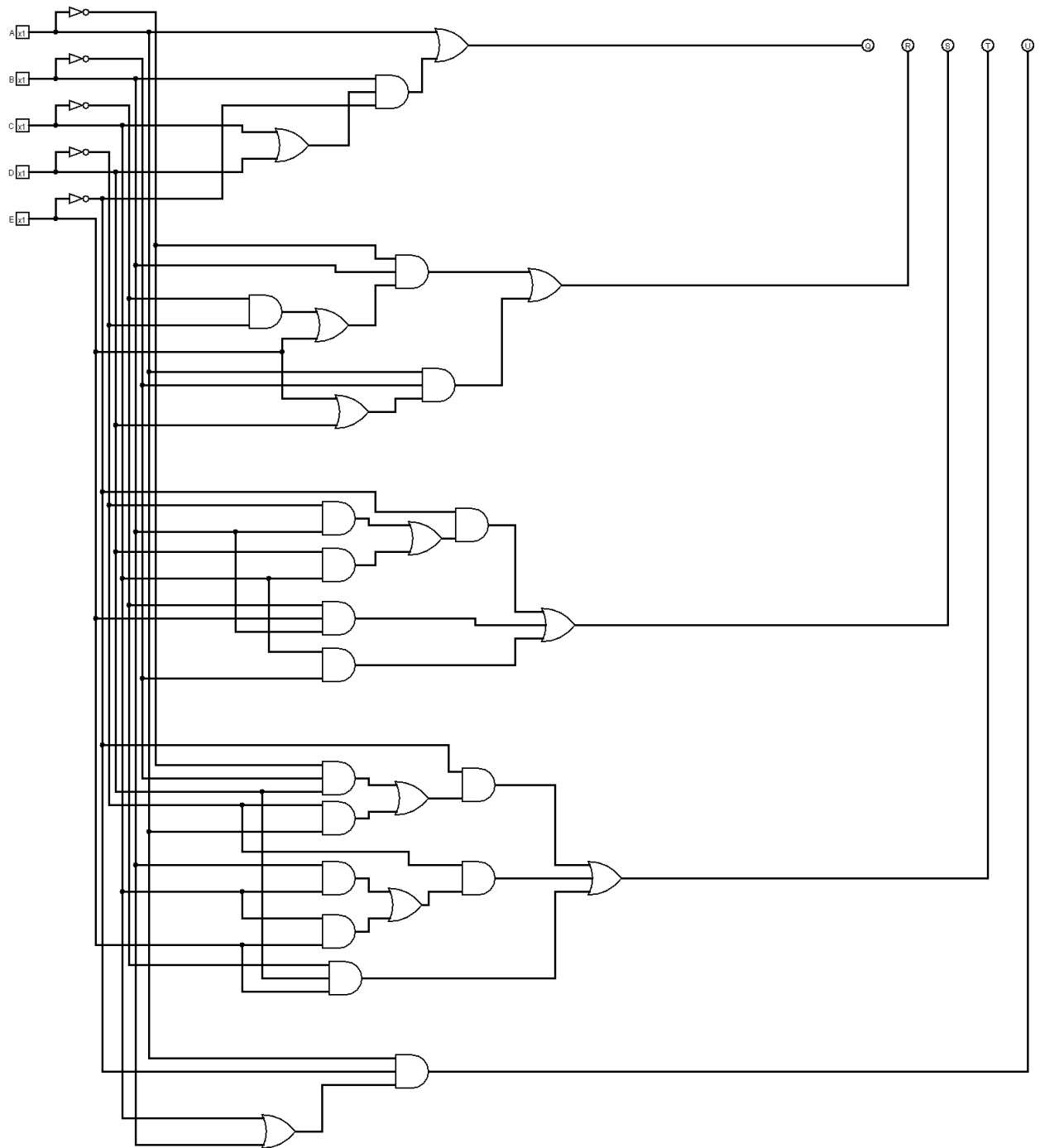

## NAND Circuit:

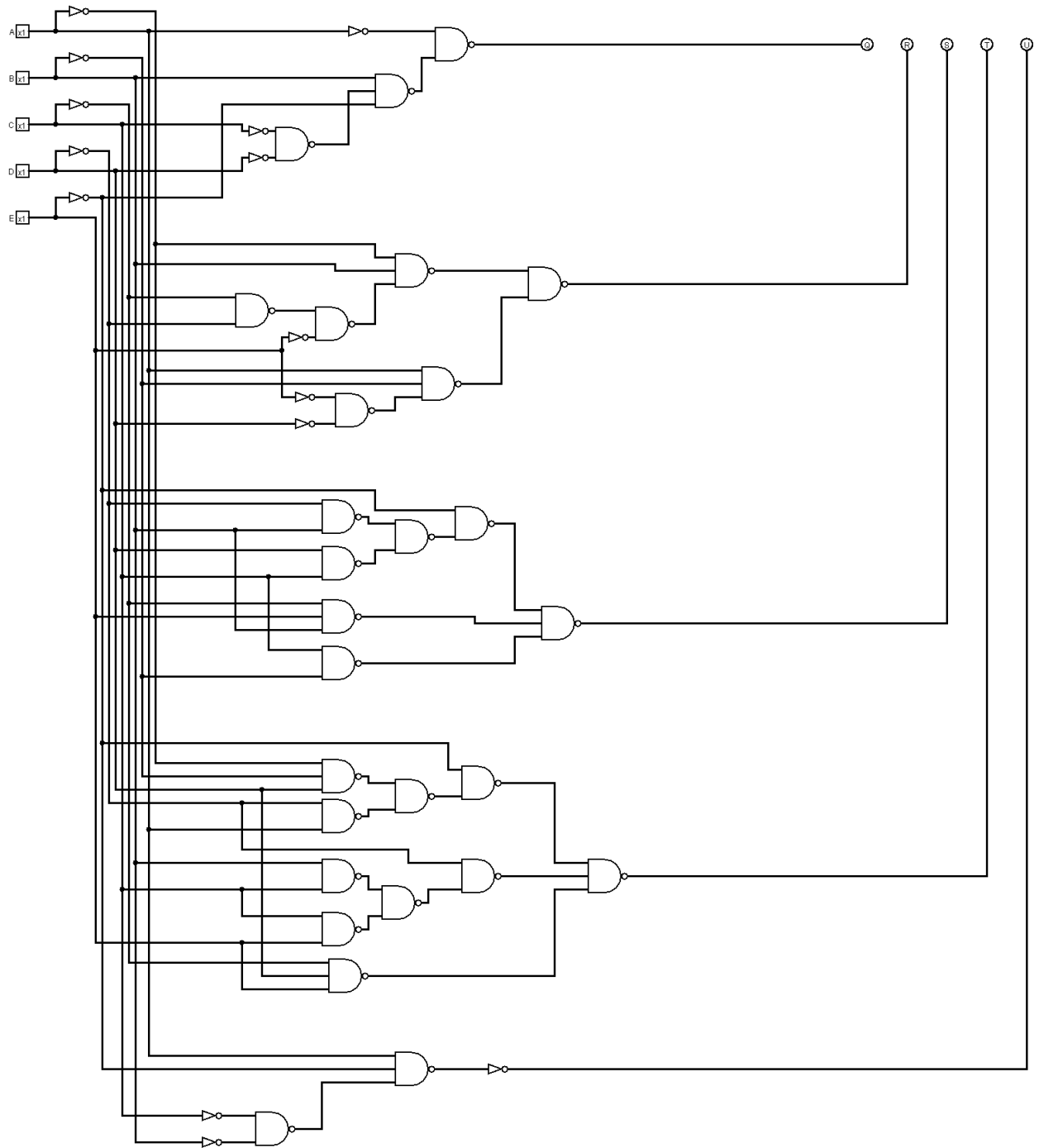

### NOR Circuit:

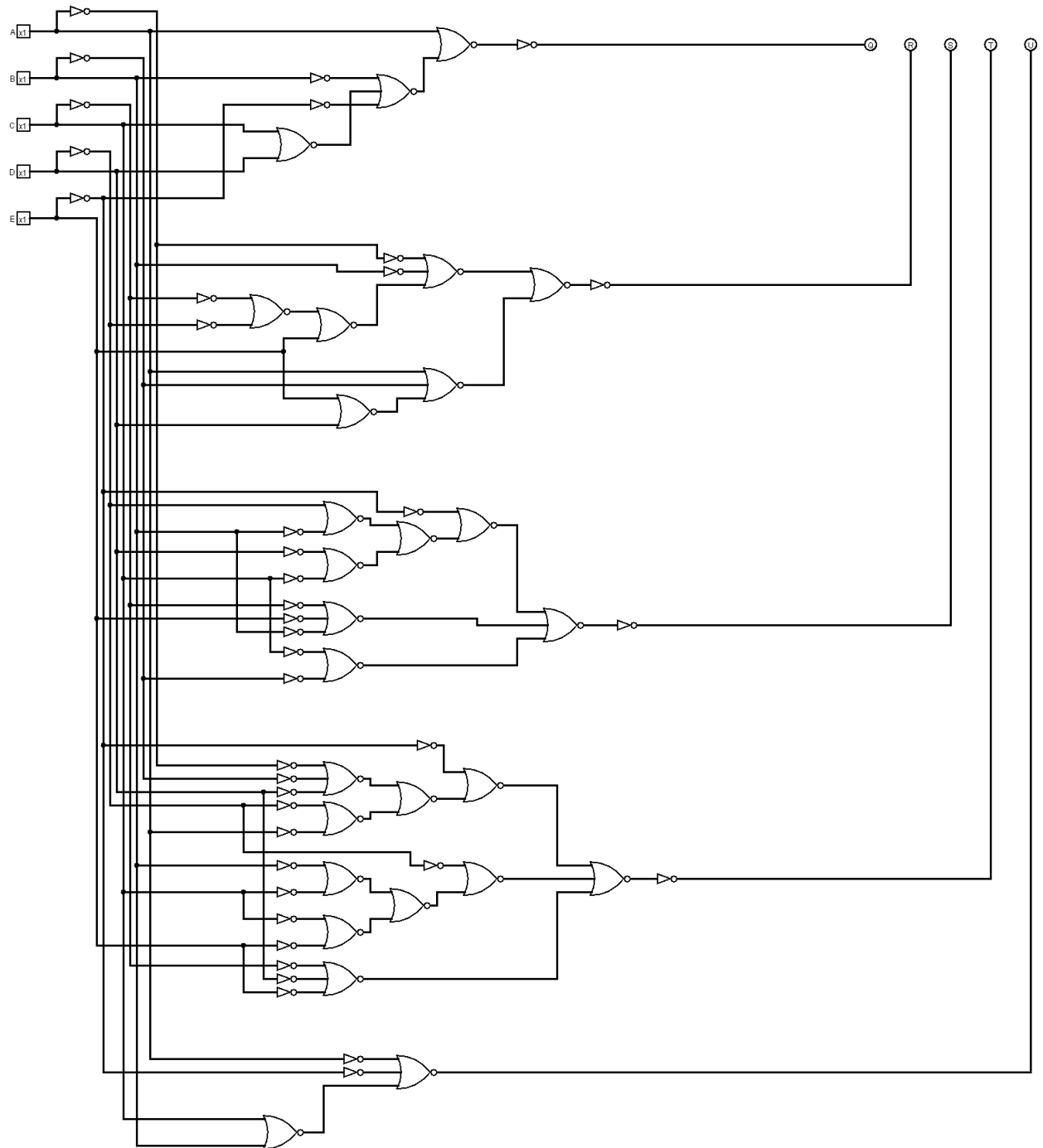

## Tinkercad Circuit:

